

# Digital Logic Systems

## Recitation 7: Foundation of Combinational Circuits, Trees, Masks

Guy Even    Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

April 30, 2019

The building blocks of combinational circuits:

- Combinational gates
- Wires and nets
- I/O ports

# Wires and nets

A **wire** is a connection between two terminals (e.g., an output of one gate and an input of another gate). In the zero-noise model, the signals at both ends of a wire are identical.

Very often we need to connect several terminals (i.e., inputs and outputs of gates) together. We could, of course, use any set of edges (i.e., wires) that connects these terminals together. Instead of specifying how the terminals are physically connected together, we use nets.

## Definition

A **net** is a subset of terminals that are connected by wires. The **fan-out** of a net  $N$  is the number of input terminals that are contained in  $N$ .

# Example

We may draw a net in any way that we find convenient or aesthetic. The interpretation of the drawing is that terminals that are connected by lines or curves constitute a net.

 


Figure: Three equivalent nets.

# Simple nets

The following definition captures the type of nets we would like to use. We call these nets *simple*.

## Definition

A net  $N$  is *simple* if (i)  $N$  is fed by exactly one output terminal, and (ii)  $N$  feeds at least one input terminal.

A simple net  $N$  that is fed by the output terminal  $t$  and feeds the input terminals  $\{t_i\}_{i \in I}$  can be modeled by the wires  $\{w_i\}_{i \in I}$ . Each wire  $w_i$  connects  $t$  and  $t_i$ . In fact, since information flows in one direction, we may regard each wire  $w_i$  as a directed edge  $t \rightarrow t_i$ . To simplify the discussion, we model simple nets by a “star” of wires emanating from a common output terminal.

Each such wire connects an output terminal of a gate to input terminal of a gate. Thus, a full description of a wire is of the form  $(g_1, t_1) \rightarrow (g_2, t_2)$ , where  $t_1$  is an output terminal of gate  $g_1$  and  $t_2$  is an input terminal of gate  $g_2$ .

# Input/Output gates


## Definition (input and output gates)

An *input gate* is a gate with zero inputs and a single output.

An *output gate* is a gate with one input and zero outputs.



Input Gate

 

Output Gate

- Inputs from the “external world” are fed to a circuit via input gates.
- Outputs to the “external world” are fed by the circuit via output gates.
- an input gate is labeled  $(IN, x_i)$ , where  $x_i$  is the name of the signal along the wire that emanates from it.
- an output gate is labeled  $(OUT, y_i)$ , where  $y_i$  is the name of the signal along the wire that enters it.

# Combinational Gates

- **inputs and outputs** of a gate are often referred to as *terminals*, *ports*, or even *pins*.
- **fan-in** of a gate  $g$  = number of input terminals of  $g$  (i.e., the number of bits in the domain of the Boolean function that specifies the functionality of  $g$ ).
- **The basic gates** that we consider are: inverter (NOT-gate), OR-gate, NOR-gate, AND-gate, NAND-gate, XOR-gate, NXOR-gate, multiplexer (MUX). All these gates have a single output.
- basic gates have constant fan-in (1 for inverter, 3 for MUX only, 2 for all the others). We usually assume that these basic gates have the same constant  $t_{pd}$ . This assumption is not precise.
- fan-out  $\neq$  the number of output ports.

# Combinational Circuit - definition

For simplicity, we assume that  $\Gamma$  contains combinational gates with a single output terminal, two input terminals, and implement commutative Boolean functions.

Let  $IO$  denote a library that contains two special types of gates: input-gates  $(IN, x_i)$  and output-gates  $(OUT, y_j)$ .

## Definition

A **combinational circuit**  $C$  is a pair  $(G, \pi)$ , where  $G = (V, E)$  is a directed acyclic graph and  $\pi : V \rightarrow \Gamma \cup IO$  is a labeling function such that:

- 1  $\pi(v) \in IO$  iff  $v$  is a source or a sink in  $G$ .
- 2 For every vertex  $v$ , the in-degree of  $v$  equals the fan-in of  $\pi(v)$ .
- 3 The restriction of  $\pi$  to sources and sinks is one-to-one. (Namely, the names of input-gates and output-gates are distinct.)



We judge the combinational circuits by:

- **Cost** - sum of all the gates' costs
- **Propagation Delay** - sum of  $t_{pd}$  of all components along the critical path

- Let  $C = (G, \pi)$  denote a combinational circuit where  $G = (V, E)$  is a directed graph and  $\pi : V \rightarrow \Gamma \cup IO$  is a labeling.
- Let  $c : \Gamma \cup IO \rightarrow \mathbb{R}^{\geq 0}$  denote a cost function. Usually, input-gates and output-gates have zero cost.

## Definition

The cost of  $C$  is defined by

$$c(C) \triangleq \sum_{v \in V} c(\pi(v)).$$

# Propagation delay

The propagation delays  $t_{pd}(v)$  are computed by Algorithm  $\text{SIM}(C, \vec{x})$ .

## Definition

The propagation delay of  $C$  is defined by

$$t_{pd}(C) \triangleq \max_{v \in V} t_{pd}(v).$$

We often refer to the propagation delay of a combinational circuit as its **depth** or simply its **delay**.

## Definition

The propagation delay of a path  $p$  in  $G$  is defined as

$$t_{pd}(p) \triangleq \sum_{v \in p} t_{pd}(\pi(v)).$$

## Example


Consider an and-gate with inputs  $x_1(t)$  and  $x_2(t)$  and an output  $y(t)$ . Given:  $t_{pd} = 2$ ,  $t_{cont} = 0$ . seconds. (All time units are in seconds in this example, so units will not be mentioned anymore in this example).

# Propagation delay example (skipped in lecture slides 10-11)
 
## Example

Consider an and-gate with inputs  $x_1(t)$  and  $x_2(t)$  and an output  $y(t)$ . Given:  $t_{pd} = 2$ ,  $t_{cont} = 0$ . seconds. (All time units are in seconds in this example, so units will not be mentioned anymore in this example).

The inputs equal 1 during the interval  $[100, 109]$ . When is the gate consistent?




# Propagation delay example (skipped in lecture slides 10-11)
 
## Example

Consider an and-gate with inputs  $x_1(t)$  and  $x_2(t)$  and an output  $y(t)$ . Given:  $t_{pd} = 2$ ,  $t_{cont} = 0$ . seconds. (All time units are in seconds in this example, so units will not be mentioned anymore in this example).

The inputs equal 1 during the interval  $[100, 109]$ . When is the gate consistent?  $y(t) = 1$  in the interval  $[102, 109]$




# Propagation delay example (skipped in lecture slides 10-11)
 
## Example

Consider an and-gate with inputs  $x_1(t)$  and  $x_2(t)$  and an output  $y(t)$ . Given:  $t_{pd} = 2$ ,  $t_{cont} = 0$ . seconds. (All time units are in seconds in this example, so units will not be mentioned anymore in this example).

$x_1(t) = 1$  during the interval  $(109, 115]$ ,  $x_2(t)$  = non-logical during the interval  $(109, 110)$ , and  $x_2(t) = 0$  during the interval  $[110, 115]$ . What can we say about  $y(t)$ ?



# Propagation delay example (skipped in lecture slides 10-11)

## Example

Consider an and-gate with inputs  $x_1(t)$  and  $x_2(t)$  and an output  $y(t)$ . Given:  $t_{pd} = 2$ ,  $t_{cont} = 0$ . seconds. (All time units are in seconds in this example, so units will not be mentioned anymore in this example).

$x_1(t) = 1$  during the interval  $(109, 115]$ ,  $x_2(t) = \text{non-logical}$  during the interval  $(109, 110)$ , and  $x_2(t) = 0$  during the interval  $[110, 115]$ . What can we say about  $y(t)$ ? = 0 in  $t \in [112, 115]$






# Propagation delay example (skipped in lecture slides 10-11)
 
## Example

Consider an and-gate with inputs  $x_1(t)$  and  $x_2(t)$  and an output  $y(t)$ . Given:  $t_{pd} = 2$ ,  $t_{cont} = 0$ . seconds. (All time units are in seconds in this example, so units will not be mentioned anymore in this example).

$x_2(t)$  remains stable during the interval  $[110, 120]$ ,  $x_1(t)$  becomes non-logical during the interval  $(115, 116)$ , and  $x_1(t)$  equals 1 again during the interval  $[116, 120]$ .  $y(t) =$




# Propagation delay example (skipped in lecture slides 10-11)
 
## Example

Consider an and-gate with inputs  $x_1(t)$  and  $x_2(t)$  and an output  $y(t)$ . Given:  $t_{pd} = 2$ ,  $t_{cont} = 0$ . seconds. (All time units are in seconds in this example, so units will not be mentioned anymore in this example).

$x_2(t)$  remains stable during the interval  $[110, 120]$ ,  $x_1(t)$  becomes non-logical during the interval  $(115, 116)$ , and  $x_1(t)$  equals 1 again during the interval  $[116, 120]$ .  $y(t) = 0$  in  $t \in [118, 120]$



Algorithm  $\text{SIM}(C, \vec{x})$  computes the largest delay of a path in  $G$ .

## Claim (9)

$$t_{pd}(C) = \max \{ t_{pd}(p) \mid p \text{ is a path in } G \}$$

## Definition

Let  $C = (G, \pi)$  denote a combinational circuit. A path  $p$  in  $G$  is **critical** if  $t_{pd}(p) = t_{pd}(C)$ .

We focus on critical paths that are maximal (i.e., cannot be further augmented). This means that maximal critical paths begin in an input-gate and end in an output-gate.

# SIM - Algorithm for a simulation of a combinational circuit

---

**Algorithm 11.1**  $\text{SIM}(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .

---

$(v_1, v_2, \dots, v_n) \leftarrow TS(DG(C))$  {topological sorting of  $DG(C)$ }

For  $i = 1$  to  $n$  do

    switch  $\text{deg}_{in}(v_i)$

    case  $\text{deg}_{in}(v_i) = 0$ :    $\{\pi(v_i) = (\text{IN}, x_j)\}$

- Let  $x_j$  denote the name of  $v_i$  before topological sorting.
- Set  $f_{v_i}(\vec{x}) \triangleq x_j$  and  $t_{pd}(v_i) \triangleq 0$ .

    case  $\text{deg}_{in}(v_i) = 1$ :

        If  $\{\pi(v_i) = \text{NOT}\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

        If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

    case  $\text{deg}_{in}(v_i) = 2$ :

- Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .

# Example - SIM algorithm

Consider the following circuit

**Algorithm 11.1**  $\text{SIM}(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .

$(v_1, v_2, \dots, v_n) \leftarrow \text{TS}(\text{DG}(C))$

For  $i = 1$  to  $n$  do

    switch  $\text{deg}_{in}(v_i)$

    case  $\text{deg}_{in}(v_i) = 0$ :     $\{\pi(v_i) = (\text{IN}, x_j)\}$

- Let  $x_j$  denote the name of  $v_i$  before topological sorting.
- Set  $f_{v_i}(\vec{x}) \triangleq x_j$  and  $t_{pd}(v_i) \triangleq 0$ .

    case  $\text{deg}_{in}(v_i) = 1$ :

        If  $\{\pi(v_i) = \text{NOT}\}$ , then


- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

        If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

    case  $\text{deg}_{in}(v_i) = 2$ :

 - Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .



# Example - SIM algorithm

## First step - run topological sorting

**Algorithm 11.1**  $\text{SIM}(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .

$(v_1, v_2, \dots, v_n) \leftarrow \text{TS}(\text{DG}(C))$

For  $i = 1$  to  $n$  do

    switch  $\text{deg}_{in}(v_i)$

    case  $\text{deg}_{in}(v_i) = 0$ :     $\{\pi(v_i) = (\text{IN}, x_j)\}$

- Let  $x_j$  denote the name of  $v_i$  before topological sorting.
- Set  $f_{v_i}(\vec{x}) \hat{=} x_j$  and  $t_{pd}(v_i) \hat{=} 0$ .

    case  $\text{deg}_{in}(v_i) = 1$ :

        If  $\{\pi(v_i) = \text{NOT}\}$ , then


- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

        If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

    case  $\text{deg}_{in}(v_i) = 2$ :

 - Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .



# Example - SIM algorithm

Begin iterating according to topological order

**Algorithm 11.1**  $\text{SIM}(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .

$(v_1, v_2, \dots, v_n) \leftarrow \text{TS}(\text{DG}(C))$

For  $i = 1$  to  $n$  do  $i=1$

switch  $\text{deg}_{in}(v_i)$

case  $\text{deg}_{in}(v_i) = 0$ :  $\{\pi(v_i) = (\text{IN}, x_j)\}$

- Let  $x_j$  denote the name of  $v_i$  before topological sorting.
- Set  $f_{v_i}(\vec{x}) \triangleq x_j$  and  $t_{pd}(v_i) \triangleq 0$ .

case  $\text{deg}_{in}(v_i) = 1$ :

If  $\{\pi(v_i) = \text{NOT}\}$ , then


- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

case  $\text{deg}_{in}(v_i) = 2$ :

 - Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .



# Example - SIM algorithm

Input x1 is evaluated as a zeros-delay identity function

**Algorithm 11.1**  $SIM(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .

$(v_1, v_2, \dots, v_n) \leftarrow TS(DG(C))$

For  $i = 1$  to  $n$  do  $i=1$

switch  $deg_{in}(v_i)$

case  $deg_{in}(v_i) = 0$ :  $\{\pi(v_i) = (IN, x_j)\}$

- Let  $x_j$  denote the name of  $v_i$  before topological sorting.
- Set  $f_{v_i}(\vec{x}) \triangleq x_j$  and  $t_{pd}(v_i) \triangleq 0$ .

case  $deg_{in}(v_i) = 1$ :

If  $\{\pi(v_i) = \text{NOT}\}$ , then


- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

case  $deg_{in}(v_i) = 2$ :

 - Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .



input vector=010



# Example - SIM algorithm

Input x2 is evaluated as a zeros-delay identity function

**Algorithm 11.1**  $\text{SIM}(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .

$(v_1, v_2, \dots, v_n) \leftarrow \text{TS}(\text{DG}(C))$

For  $i = 1$  to  $n$  do  $i=2$

switch  $\text{deg}_{in}(v_i)$

case  $\text{deg}_{in}(v_i) = 0$ :  $\{\pi(v_i) = (\text{IN}, x_j)\}$

- Let  $x_j$  denote the name of  $v_i$  before topological sorting.
- Set  $f_{v_i}(\vec{x}) \triangleq x_j$  and  $t_{pd}(v_i) \triangleq 0$ .

case  $\text{deg}_{in}(v_i) = 1$ :

If  $\{\pi(v_i) = \text{NOT}\}$ , then


- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

case  $\text{deg}_{in}(v_i) = 2$ :

 - Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .



input vector=010

# Example - SIM algorithm

Input x3 is evaluated as a zeros-delay identity function

**Algorithm 11.1**  $SIM(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .

$(v_1, v_2, \dots, v_n) \leftarrow TS(DG(C))$

For  $i = 1$  to  $n$  do  $i=3$

switch  $deg_{in}(v_i)$

case  $deg_{in}(v_i) = 0$ :  $\{\pi(v_i) = (IN, x_j)\}$

- Let  $x_j$  denote the name of  $v_i$  before topological sorting.
- Set  $f_{v_i}(\vec{x}) \hat{=} x_j$  and  $t_{pd}(v_i) \hat{=} 0$ .

case  $deg_{in}(v_i) = 1$ :

If  $\{\pi(v_i) = \text{NOT}\}$ , then


- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

case  $deg_{in}(v_i) = 2$ :

 - Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .



input vector=010

# Example - SIM algorithm

## Inverter is evaluated

**Algorithm 11.1**  $\text{SIM}(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .

$(v_1, v_2, \dots, v_n) \leftarrow \text{TS}(\text{DG}(C))$

For  $i = 1$  to  $n$  do  $i=4$

switch  $\text{deg}_{in}(v_i)$

case  $\text{deg}_{in}(v_i) = 0$ :  $\{\pi(v_i) = (\text{IN}, x_j)\}$

- Let  $x_j$  denote the name of  $v_i$  before topological sorting.
- Set  $f_{v_i}(\vec{x}) \hat{=} x_j$  and  $t_{pd}(v_i) \hat{=} 0$ .

case  $\text{deg}_{in}(v_i) = 1$ :

If  $\{\pi(v_i) = \text{NOT}\}$ , then


- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

case  $\text{deg}_{in}(v_i) = 2$ :

 - Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .



# Example - SIM algorithm

## AND2 gate is evaluated

**Algorithm 11.1**  $\text{SIM}(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .

$(v_1, v_2, \dots, v_n) \leftarrow \text{TS}(\text{DG}(C))$

For  $i = 1$  to  $n$  do i=5

    switch  $\text{deg}_{in}(v_i)$

    case  $\text{deg}_{in}(v_i) = 0$ :  $\{\pi(v_i) = (\text{IN}, x_j)\}$

- Let  $x_j$  denote the name of  $v_i$  before topological sorting.
- Set  $f_{v_i}(\vec{x}) \hat{=} x_j$  and  $t_{pd}(v_i) \hat{=} 0$ .

    case  $\text{deg}_{in}(v_i) = 1$ :

        If  $\{\pi(v_i) = \text{NOT}\}$ , then


- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

        If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

case  $\text{deg}_{in}(v_i) = 2$ :

 
- Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .



# Example - SIM algorithm
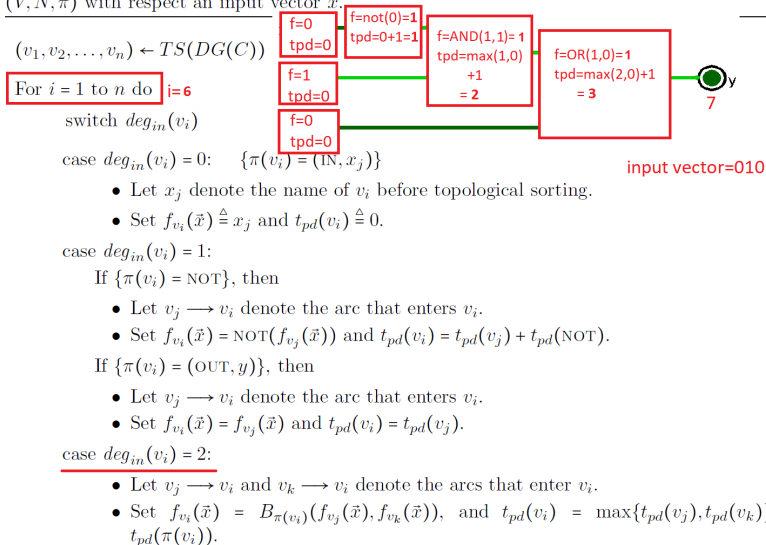
## OR2 gate is evaluated


**Algorithm 11.1**  $SIM(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .


 
# Example - SIM algorithm

Output gate  $y$  is evaluated as a zero delay identity function

**Algorithm 11.1**  $\text{SIM}(C, \vec{x})$  - An algorithm for simulating the combinational circuit  $C = (V, N, \pi)$  with respect an input vector  $\vec{x}$ .



- Let  $x_j$  denote the name of  $v_i$  before topological sorting.

- Set  $f_{v_i}(\vec{x}) \triangleq x_j$  and  $t_{pd}(v_i) \triangleq 0$ .

case  $\text{deg}_{in}(v_i) = 1$ :

If  $\{\pi(v_i) = \text{NOT}\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = \text{NOT}(f_{v_j}(\vec{x}))$  and  $t_{pd}(v_i) = t_{pd}(v_j) + t_{pd}(\text{NOT})$ .

If  $\{\pi(v_i) = (\text{OUT}, y)\}$ , then

- Let  $v_j \rightarrow v_i$  denote the arc that enters  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = f_{v_j}(\vec{x})$  and  $t_{pd}(v_i) = t_{pd}(v_j)$ .

case  $\text{deg}_{in}(v_i) = 2$ :

- Let  $v_j \rightarrow v_i$  and  $v_k \rightarrow v_i$  denote the arcs that enter  $v_i$ .
- Set  $f_{v_i}(\vec{x}) = B_{\pi(v_i)}(f_{v_j}(\vec{x}), f_{v_k}(\vec{x}))$ , and  $t_{pd}(v_i) = \max\{t_{pd}(v_j), t_{pd}(v_k)\} + t_{pd}(\pi(v_i))$ .

## Question 1: How hard is the critical path computation?

Recall Claim 9

Claim (9)

$$t_{pd}(C) = \max \{ t_{pd}(p) \mid p \text{ is a path in } G \}$$

The number of paths can be exponential in  $n$ . Does this mean that we cannot compute the propagation delay of a combinational circuit in linear time?

**Answer:** Homework

## Question 2 - A common counting problem

### Example


One wants to have all the possible couples of  $x_i, x_j$  to go through a XOR gate and reach a  $y_k$ . What would be the cost of such a circuit? What is the propagation delay?



## Question 2 - A common counting problem
 
### Example


One wants to have all the possible couples of  $x_i, x_j$  to go through a XOR gate and reach a  $y_k$ . What would be the cost of such a circuit? What is the propagation delay?



## Question 2 - A common counting problem
 
### Example


One wants to have all the possible couples of  $x_i, x_j$  to go through a XOR gate and reach a  $y_k$ . What would be the cost of such a circuit? What is the propagation delay?



## Question 2 - A common counting problem
 
### Example

One wants to have all the possible couples of  $x_i, x_j$  to go through a XOR gate and reach a  $y_k$ . What would be the cost of such a circuit? What is the propagation delay?



All the gates are summed up to:

$$c(n) = \sum_{i=0}^{n-1} i \quad \underbrace{=}_{\text{arithmetic series}} \quad 0 \cdot n + 1 \cdot \frac{(n-1) \cdot n}{2} = \Theta(n^2)$$

# Associative Boolean functions

## Definition

A Boolean function  $f : \{0, 1\}^2 \rightarrow \{0, 1\}$  is *associative* if

$$f(f(\sigma_1, \sigma_2), \sigma_3) = f(\sigma_1, f(\sigma_2, \sigma_3)),$$

for every  $\sigma_1, \sigma_2, \sigma_3 \in \{0, 1\}$ .

If  $f(x_1, x_2)$  is an associative Boolean function, then one could define  $f_n$  in many equivalent ways, as summarized in the following claim.

## Claim

If  $f : \{0, 1\}^2 \rightarrow \{0, 1\}$  is an associative Boolean function, then

$$f_n(x_1, x_2, \dots, x_n) = f(f_{n-k}(x_1, \dots, x_{n-k}), f_k(x_{n-k+1}, \dots, x_n)),$$

for every  $n \geq 2$  and  $k \in [1, n-1]$ .

# Associative Boolean functions

Among the 16 existing binary ( $n = 2$  variables) Boolean operators - 8 which are *associative*:

- ①  $f(x, y) = \text{AND}(x, y)$
- ②  $f(x, y) = \text{OR}(x, y)$
- ③  $f(x, y) = \text{XOR}(x, y)$
- ④  $f(x, y) = \text{NXOR}(x, y)$
- ⑤  $f(x, y) = x$
- ⑥  $f(x, y) = y$
- ⑦  $f(x, y) = 1$
- ⑧  $f(x, y) = 0$

# Associative Boolean functions

Among the 16 existing binary ( $n = 2$  variables) Boolean operators - 8 which are *associative*:

- ①  $f(x, y) = \text{AND}(x, y)$
- ②  $f(x, y) = \text{OR}(x, y)$
- ③  $f(x, y) = \text{XOR}(x, y)$
- ④  $f(x, y) = \text{NXOR}(x, y)$
- ⑤  $f(x, y) = x$
- ⑥  $f(x, y) = y$
- ⑦  $f(x, y) = 1$
- ⑧  $f(x, y) = 0$

## Important Remark

For higher number of inputs  $n > 2$ , these functions can be implemented using by a **tree-structured** combinational circuit.

# Associative Boolean functions

Among the 16 existing binary ( $n = 2$  variables) Boolean operators - 8 which are *associative*:

- ①  $f(x, y) = \text{AND}(x, y)$
- ②  $f(x, y) = \text{OR}(x, y)$
- ③  $f(x, y) = \text{XOR}(x, y)$
- ④  $f(x, y) = \text{NXOR}(x, y)$
- ⑤  $f(x, y) = x$
- ⑥  $f(x, y) = y$
- ⑦  $f(x, y) = 1$
- ⑧  $f(x, y) = 0$

## Important Remark

For higher number of inputs  $n > 2$ , these functions can be implemented using by a **tree-structured** combinational circuit.

## Example

OR-Tree( $n$ ), AND-Tree( $n$ ), XOR-Tree( $n$ ). Where  $n$  is # inputs

# Trees can have large delay

- A tree with  $n$  inputs can have a **linear delay**  $\Theta(n)$  if not balanced properly.



# Trees can have large delay

- A tree with  $n$  inputs can have a **linear delay**  $\Theta(n)$  if not balanced properly.
- We want to construct trees with **logarithmic delay**  $\Theta(\log(n))$ .

# Trees can have large delay

- A tree with  $n$  inputs can have a **linear delay**  $\Theta(n)$  if not balanced properly.
- We want to construct trees with **logarithmic delay**  $\Theta(\log(n))$ .
- Solution: **Balanced-Tree( $n$ )** algorithm:
  - 1 Case of  $n = 1$  is trivial, just return the variable itself.
  - 2 If  $n \geq 2$  then
    - 1 let  $a, b$  be a **balanced partition** of  $n$
    - 2  $T_a^* = \text{Balanced-Tree}(a)$
    - 3  $T_b^* = \text{Balanced-Tree}(b)$
    - 4 Connect the roots of  $T_a^*, T_b^*$  to a new (fan-in=2) root.

# Balanced partitions

## Definition

Two positive integers  $a, b$  are a **balanced partition** of  $n$  if:

- 1  $a + b = n$ , and
- 2  $\max\{\lceil \log_2 a \rceil, \lceil \log_2 b \rceil\} \leq \lceil \log_2 n \rceil - 1$ .

## Claim (This is how you pick balanced $(a,b)$ pairs)

*If  $n = 2^k - r$ , where  $0 \leq r < 2^{k-1}$ , then the set of balanced partitions is*

$$P \triangleq \{(a, b) \mid 2^{k-1} - r \leq a \leq 2^{k-1} \text{ and } b = n - a\}.$$

## Corollary (12.10)

*The propagation delay of a balanced OR-tree( $n$ ) is  $\lceil \log_2 n \rceil \cdot t_{pd}(\text{OR})$ .*

# Bitwise operations

Logic instructions are commonly used to set (turn on) or clear (reset, turn off) individual bits within a word without affecting other bits.

## AND-mask

By ANDing a value with a deliberately designed constant, called a “bit mask” we can **clear/preserve** specific bits.

Zeros in the mask clear the corresponding value.

Ones in the mask preserve the corresponding value.

value 10010100

mask 00001111

---

result 00000100

# Masks and bitwise operations

## OR-mask

OR operation is used to **preserve/set** bits.

Zeros in the mask preserve the corresponding value.

Ones in the mask set the corresponding value to 1.

value 10010100

mask 00001111

---

result 10011111

## XOR-mask

An XOR can be used to **preserve/negate** specific bits.

Zeros in the mask preserve the corresponding value.

Ones in the mask flip the corresponding value.

value 10010100

mask 00001111

---

result 10011011

## Example

$PB(n)$  is a combinational circuit defined as follows:

**Input:**  $x, m \in \{0, 1\}^n$

**Output:**  $y \in \{0, 1\}$ .

**Functionality:**

$$y \triangleq OR(\{x_i | m_i = 1\})$$

Note:  $OR(\emptyset) \triangleq 0$

# Masks - Example

## Example

$PB(n)$  is a combinational circuit defined as follows:


**Input:**  $x, m \in \{0, 1\}^n$

**Output:**  $y \in \{0, 1\}$ .

**Functionality:**

$$y \triangleq OR(\{x_i | m_i = 1\})$$

Note:  $OR(\emptyset) \triangleq 0$

 

# Circuit parameters vs inputs

## Example

Consider the following circuit  $\text{Toy}(n)$

**Input:**  $x \in \{0, 1\}^n$

**Output:**  $y \in \{0, 1\}$ .

**Functionality:** Let  $p = \langle x[n-1:0] \rangle$ . The output  $y$  respects the following:

$$y = 1 \Leftrightarrow p = 2^{n-1}$$

$n$  is the  $\text{Toy}(n)$ 's parameter

It is a hardwired constant of a particular circuit. It cannot be changed during the circuit's operation, but can be used as a design parameter.

$p$  is the  $\text{Toy}(n)$ 's input value

It changes during the operation of the circuit, as a function of the input  $x$ . Cannot be used as a design parameter.