

Digital Logic Systems

Recitation 8: Lower Bounds on cost and delay, Multiplexers, Decoders, Encoders

Guy Even Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

May 6, 2019

When does a function depend on an input?

Definition

A Boolean function $f : \{0, 1\}^n \rightarrow \{0, 1\}$ **depends** on its i^{th} input if

$$f_{\upharpoonright x_i=0} \neq f_{\upharpoonright x_i=1}.$$

Example

Consider the Boolean function $f(\vec{x}) = \text{XOR}_2(x_1, x_2)$. The function f depends on the i^{th} input for $i = 2$. Indeed, $f_{\upharpoonright x_2=1}(x_1) = \text{NOT}(x_1)$ and $f_{\upharpoonright x_2=0}(x_1) = x_1$.

The cone of a function

Definition (Cone of a Boolean function)

The **cone** of a Boolean function $f : \{0, 1\}^n \rightarrow \{0, 1\}$ is defined by

$$\text{cone}(f) \triangleq \{i : f_{\upharpoonright x_i=0} \neq f_{\upharpoonright x_i=1}\}.$$

Alternative Definition (Cone of a Boolean function)

Let $f : \{0, 1\}^n \rightarrow \{0, 1\}^k$ denote a Boolean function. Then,

$$i \in \text{cone}(f) \iff \exists \vec{v} \in \{0, 1\}^n : f(\vec{v}) \neq f(\text{flip}_i(\vec{v})).$$

Cone of a function f is a set of all the indices that f depends on.

Example

The cone of the Boolean function $f(\vec{x}) = \text{XOR}_2(x_1, x_2)$ equals $\{1, 2\}$ because XOR depends on both inputs.

Example

Consider the following Boolean function:

$$f(\vec{x}) = \begin{cases} 0 & \text{if } \sum_i x_i < 3 \\ 1 & \text{otherwise.} \end{cases}$$

Suppose that one reveals the input bits one by one. As soon as 3 ones are revealed, one can determine the value of $f(\vec{x})$.

Nevertheless, the function $f(\vec{x})$ depends on all its inputs, and hence, $\text{cone}(f) = \{1, \dots, n\}$.

Lower Bound Theorems

Theorem

Let C denote a combinational circuit that implements a Boolean function $f : \{0,1\}^n \rightarrow \{0,1\}$. If the fan-in of every gate in C is at most 2, then

$$c(C) \geq |\text{cone}(f)| - 1.$$

Theorem

Let $C = (G, \pi)$ denote a combinational circuit that implements a non-constant Boolean function $f : \{0,1\}^n \rightarrow \{0,1\}$. If the fan-in of every gate in C is at most k , then

$$t_{pd}(C) \geq \log_k |\text{cone}(f)|.$$

The lower bounds are on the **function** (based on the cone of your function). Whereas the actual order of growth of the design are on your design

Definition of Decoder

Definition

A **decoder with input length n** :

Input: $x[n-1:0] \in \{0,1\}^n$.

Output: $y[2^n-1:0] \in \{0,1\}^{2^n}$

Functionality:

$$y[i] \triangleq \begin{cases} 1 & \text{if } \langle \vec{x} \rangle = i \\ 0 & \text{otherwise.} \end{cases}$$

Number of outputs of a decoder is exponential in the number of inputs. Note also that exactly one bit of the output \vec{y} is set to one. Such a representation of a number is often termed **one-hot encoding** or **1-out-of- k encoding**.

Example

Consider a decoder `DECODER(3)`. On input $x = 101$, the output y equals 00100000.

An asymptotically optimal decoder design

Base case $\text{DECODER}(1)$:

The circuit $\text{DECODER}(1)$ is simply one inverter where:

$y[0] \leftarrow \text{INV}(x[0])$ and $y[1] \leftarrow x[0]$.

Reduction rule $\text{DECODER}(n)$:

We assume that we know how to design decoders with input length less than n , and design a decoder with input length n .

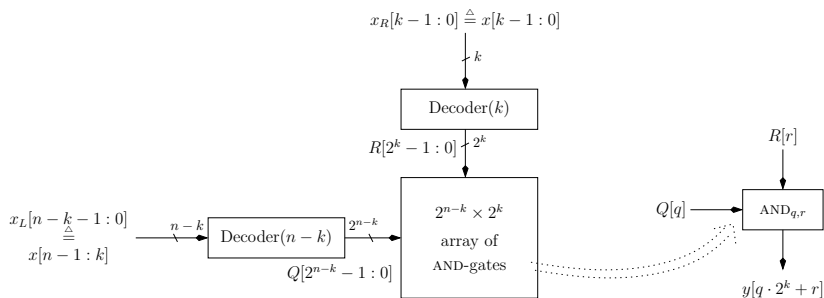


Figure: A recursive implementation of $\text{DECODER}(n)$.

Claim (Correctness)

$$y[i] = 1 \iff \langle x[n-1:0] \rangle = i.$$

Performance Analysis of Decoder

Claim


$c(n) = \Omega(2^n)$ (regardless of the value of k).

$c(n) = O(2^n)$ if $k = \lceil n/2 \rceil$.

Claim

$d(n) = \Theta(\log n)$ if $k = n/2$.

Multiplexer (MUX2 : 1)

 

Definition

A MUX-gate is a combinational gate that has three inputs $D[0]$, $D[1]$, S and one output Y . The functionality is defined by

$$Y = \begin{cases} D[0] & \text{if } S = 0 \\ D[1] & \text{if } S = 1. \end{cases}$$

Note that we could have used the shorter expression $Y = D[S]$ to define the functionality of a MUX-gate.

$(n:1)$ -MUX selects on bit out of n

Definition

An $(n:1)$ -MUX is a combinational circuit defined as follows:

Input: **data input** $D[n-1:0]$ and **select input** $S[k-1:0]$
where $k = \lceil \log_2 n \rceil$.

Output: $Y \in \{0, 1\}$.

Functionality:

$$Y = D[\langle \vec{S} \rangle].$$

To simplify the discussion, we will assume in this chapter that n is a power of 2, namely, $n = 2^k$.


Example

Let $n = 4$ and $D[3:0] = 0101$. If $S[1:0] = 00$, then $Y = D[0] = 1$.
If $S[1:0] = 01$, then $Y = D[1] = 0$.

We describe two implementations of $(n:1)$ -MUX.

- Decoder based - in the recitation (modular design).
- Tree based - in the lecture (recursive).

Decoder based $(n:1)$ -MUX

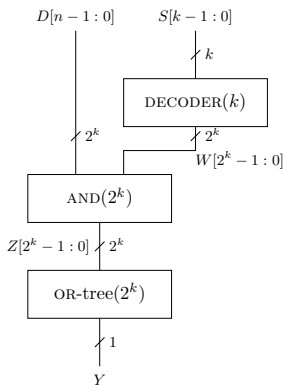


Claim

The $(n:1)$ -MUX design is correct.

Claim

The cost of the $(n:1)$ -MUX design is $\Theta(n)$.

Decoder based $(n:1)$ -MUX - delay

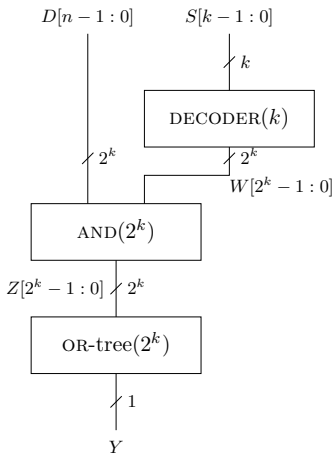

Claim

The delay of the $(n:1)$ -MUX design is $\Theta(\log n)$.

Encoder circuit - definition

Definition

An **encoder** with input length 2^n and output length n is a combinational circuit that implements the Boolean function ENCODER_n .

We denote an encoder with input length 2^n and output length n by $\text{ENCODER}(n)$. An $\text{ENCODER}(n)$ can be also specified as follows:

Input: $y[2^n - 1 : 0] \in \{0, 1\}^{2^n}$.

Output: $x[n - 1 : 0] \in \{0, 1\}^n$.

Functionality: If $\text{wt}(\vec{y}) = 1$, let i denote the index such that $y[i] = 1$. In this case \vec{x} should satisfy $\langle \vec{x} \rangle = i$.
Formally:

$$\text{wt}(\vec{y}) = 1 \implies y[\langle \vec{x} \rangle] = 1.$$

ENCODER'(n) - a recursive design

For $n = 1$, is simply $x[0] \leftarrow y[1]$.

Reduction step:

$$y_L[2^{n-1} - 1 : 0] = y[2^n - 1 : 2^{n-1}]$$


$$y_R[2^{n-1} - 1 : 0] = y[2^{n-1} - 1 : 0].$$

Use two ENCODER'(n - 1) with inputs \vec{y}_L and \vec{y}_R . But,


$$wt(\vec{y}) = 1 \Rightarrow (wt(\vec{y}_L) = 0) \vee (wt(\vec{y}_R) = 0).$$

What does an encoder output when input all-zeros?

Reduction step for $\text{ENCODER}'(n)$

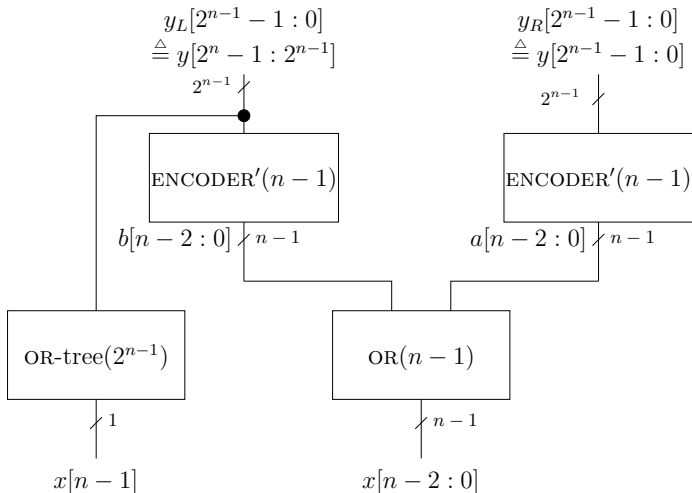

Reduction step for $\text{ENCODER}^*(n)$

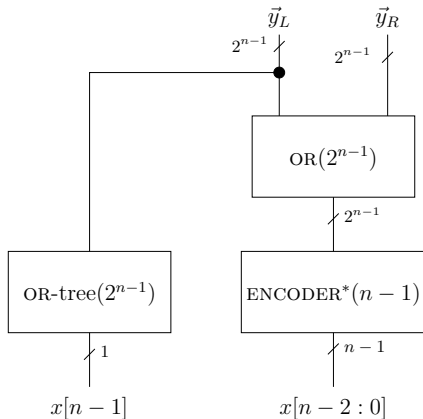

Performance Analysis of Encoder

Claim

$$c(\text{ENCODER}'(n)) = \Theta(n \cdot 2^n).$$

(asymptotically) equals the cost of the brute force design...

Claim

$$c(\text{ENCODER}^*(n)) = \Theta(2^n) \cdot c(\text{OR}).$$

Claim

$$d(\text{ENCODER}^*(n)) = n \cdot d(\text{OR}).$$

Priority Encoder - PENC(n)

A PENC(n) is a combinational circuit with input length 2^n is defined as follows.

Input: $y[2^n - 1 : 0] \in \{0, 1\}^{2^n}$.

Output: $x[n - 1 : 0] \in \{0, 1\}^n, v \in \{0, 1\}$.

Functionality: $v = 1 \Leftrightarrow y \neq 0^{2^n}$. Let i denote the highest index i such that $y[i] = 1$. In this case \vec{x} should satisfy $\langle \vec{x} \rangle = i$. Formally:

$$\vec{y} \neq 0^{2^n} \implies y[2^n - 1 : \langle \vec{x} \rangle] = 0^{2^n - 1 - \langle \vec{x} \rangle} \circ 1.$$

In other words

Priority encoder deals with situation where **more than one input is active**. The output will encode the input index with the higher “priority”.

Priority Encoder - PENC(n)

Table: The Truth Table of The Priority Encoder(3)

y7	y6	y5	y4	y3	y2	y1	y0	x2	x1	x0	v
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	1	d.c.	0	0	1	1
0	0	0	0	0	1	d.c.	d.c.	0	1	0	1
0	0	0	0	1	d.c.	d.c.	d.c.	0	1	1	1
0	0	0	1	d.c.	d.c.	d.c.	d.c.	1	0	0	1
0	0	1	d.c.	d.c.	d.c.	d.c.	d.c.	1	0	1	1
0	1	d.c.	d.c.	d.c.	d.c.	d.c.	d.c.	1	1	0	1
1	d.c.	d.c.	d.c.	d.c.	d.c.	d.c.	d.c.	1	1	1	1

Implementation Tips

- Use “Divide and Conquer”, similar to Tree-based-(n:1)-MUX.
- Use the “v” signal to choose between the sub-encoders

Design the following circuit

Input: $y[2^n - 1 : 0] \in \{0, 1\}^{2^n}$.

Output: $x[n - 1 : 0] \in \{0, 1\}^n$.

Functionality:

$$x[i] = OR(\{bin_n(j)[i] \mid y[j] = 1\})$$

For every $0 \leq i \leq n - 1$. Where $bin_n(j)$ is a function that return the n -bit binary string that represents j using n bits. ($bin_n : \{0, 1, \dots, 2^n - 1\} \rightarrow \{0, 1\}^n$)

Question

Design the following circuit

Input: $y[2^n - 1 : 0] \in \{0, 1\}^{2^n}$.

Output: $x[n - 1 : 0] \in \{0, 1\}^n$.

Functionality:

$$x[i] = OR(\{bin_n(j)[i] \mid y[j] = 1\})$$

For every $0 \leq i \leq n - 1$. Where $bin_n(j)$ is a function that return the n -bit binary string that represents j using n bits. ($bin_n : \{0, 1, \dots, 2^n - 1\} \rightarrow \{0, 1\}^n$)

Answer

An encoder. We were actually asked to implement an extended function of the encoder.