

Digital Logic Systems

Recitation 10: Signed Addition, Synchronous Circuits and Flip-Flops

Guy Even Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

May 20, 2019

- ① Read the forum, good question are being asked there.
- ② Check that your file is uploaded with a proper filename.

Recall - Combinational Circuits

Combinational circuits we saw (before addition)

- ① Basic combinational gates (AND2, OR2, MUX2:1,...)
- ② MUX($n:1$)
- ③ Shifters (cyclic, logical, arith.) - move input by $\langle \vec{s} \rangle$ places
- ④ Decoders n bits $\rightarrow 2^n$ bits
- ⑤ Encoders (and priority encoder) 2^n bits $\rightarrow n$ bits

Design approaches

- ① Divide and conquer - recursively split the input
- ② Flat - Usage of black boxes and smart wiring

Tips

- ① **Modularity** is the key!
- ② **Evolution** - begin with a naive design, and try improving it

We saw **3 different implementations** of binary adder

- ① RCA(n) - cheap and intuitive design, but has a linear delay
- ② CSA(n) - is slightly more expensive but as a logarithmic delay
- ③ COMP-ADDER(n) - outputs T and S. Cheaper than CSA, the delay remained logarithmic

Signed addition warm-up:

- ① We must define a representation of a **signed** integer.
- ② We must be able to implement **addition/subtraction** of signed integers.
- ③ Can we use the **same circuitry** for adding unsigned and signed integers?

Signed number representation - Two's Complement

We denote the number represented in **two's complement** representation by $A[n-1:0]$ as follows:

$$[A[n-1:0]] \triangleq -2^{n-1} \cdot A[n-1] + \langle A[n-2:0] \rangle.$$

We denote the set of signed numbers that are representable in two's complement representation using n -bit binary strings by T_n .

The Set T_n

$$T_n = \{-2^{n-1}, -2^{n-1} + 1, \dots, 2^{n-1} - 1\}.$$

Example

$T_{32} = \{-2147483648, \dots, 2147483647\}$ which should remind you of the limits of **int** variables, compiled for 32-bit machines.

Two's Complement - Sign bit, Sign extension & Negation

Claim (MSB determines the sign)

$$[A[n-1:0]] < 0 \iff A[n-1] = 1.$$

Claim (Sign-Extension)

If $A[n] = A[n-1]$, then

$$[A[n:0]] = [A[n-1:0]].$$

Corollary (Sign-Extension)

$$[A[n-1]^* \circ A[n-1:0]] = [A[n-1:0]].$$

Claim (Negation)

$$-[A[n-1:0]] = [\text{INV}(A[n-1:0])] + 1$$

Comparison between representation methods

binary string \vec{X}	$\langle \vec{X} \rangle$	2's comp	1's comp	sign-mag
000	0	0	0	+0
001	1	1	1	1
010	2	2	2	2
011	3	3	3	3
100	4	-4	-3	-0
101	5	-3	-2	-1
110	6	-2	-1	-2
111	7	-1	0	-3

- symmetric range: one's complement and sign-magnitude.
- two representations for zero: one's complement and sign-magnitude.

So far, we've defined a representation of **signed** integers and had a few observations about it.

It is now time to design the two's complement arithmetic logic.

Our design will follow the next procedure:

- 1 Define a **reduction** of two's complement to a binary addition
- 2 Detect **overflow** and the **sign** of the sum.
- 3 Construct a **signed adder** S-ADDER(n)
- 4 Extend the S-ADDER(n) to **adder/subtractor** ADD-SUB(n)

Reduction of two's comp addition to binary addition

Theorem

Let $C[n-1]$ denote the carry-bit in position $[n-1]$ associated with the binary addition described in Equation 16.1 and let

$$z \triangleq [A[n-1:0]] + [B[n-1:0]] + C[0].$$

Then,

$$C[n] - C[n-1] = 1 \quad \implies \quad z < -2^{n-1} \quad (1)$$

$$C[n-1] - C[n] = 1 \quad \implies \quad z > 2^{n-1} - 1 \quad (2)$$

$$z \in T_n \quad \iff \quad C[n] = C[n-1] \quad (3)$$

$$z \in T_n \quad \implies \quad z = [S[n-1:0]]. \quad (4)$$

Example

$[A[3:0]]$	-3	-4	-6	7
$[B[3:0]]$	-5	-5	5	1
$C[0]$	1	0	0	1
<hr/>				
$C[n]$	1	1	1	0
$C[n-1]$	1	0	1	1
$[S[n-1:0]]$	-7	7	-1	-7
z	-7	-9	-1	9

Detecting overflow

Overflow - the sum of signed numbers is not in T_n .

Definition

Let $z \triangleq [A[n-1:0]] + [B[n-1:0]] + C[0]$. The signal OVF is defined as follows:

$$\text{OVF} \triangleq \begin{cases} 1 & \text{if } z \notin T_n \\ 0 & \text{otherwise.} \end{cases}$$

the term “out-of-range” is more appropriate than “overflow” (which suggests that the sum is too big). Favor tradition...

Claim

$$\text{OVF} = \text{XOR}(C[n-1], C[n]).$$

Determining the sign of the sum

Definition

The signal `NEG` is defined as follows:

$$\text{NEG} \triangleq \begin{cases} 1 & \text{if } z < 0 \\ 0 & \text{if } z \geq 0. \end{cases}$$

brute force method:

$$\text{NEG} = \begin{cases} S[n-1] & \text{if no overflow} \\ 1 & \text{if } C[n] - C[n-1] = 1 \\ 0 & \text{if } C[n-1] - C[n] = 1. \end{cases} \quad (5)$$

Claim

The `NEG` signal determines the sign of the correct sum (z) even in case of an overflow. Its function can be expressed as follows:

$$\text{NEG} = \text{XOR}_3(A[n-1], B[n-1], C[n])$$

A two's-complement adder

Definition

A **two's-complement adder** with input length n is a combinational circuit specified as follows.

Input: $A[n-1:0], B[n-1:0] \in \{0,1\}^n$, and $C[0] \in \{0,1\}$.

Output: $S[n-1:0] \in \{0,1\}^n$ and $\text{NEG}, \text{OVF} \in \{0,1\}$.

Functionality: Define z as follows:

$$z \triangleq [A[n-1:0]] + [B[n-1:0]] + C[0].$$

The functionality is defined as follows:


$$z \in T_n \implies [S[n-1:0]] = z$$

$$z \in T_n \iff \text{OVF} = 0$$

$$z < 0 \iff \text{NEG} = 1.$$

We denote a two's-complement adder by $\text{S-ADDER}(n)$.

A two's complement adder S-ADDER(n)

 

In an arithmetic logic unit (ALU), one may use the same circuit for signed addition and unsigned addition.

A two's complement adder/subtractor

Definition

A **two's-complement adder/subtractor** with input length n is a combinational circuit specified as follows.

Input: $A[n-1:0], B[n-1:0] \in \{0,1\}^n$, and $sub \in \{0,1\}$.

Output: $S[n-1:0] \in \{0,1\}^n$ and $NEG, OVF \in \{0,1\}$.

Functionality: Define z as follows:

$$z \triangleq [A[n-1:0]] + (-1)^{sub} \cdot [B[n-1:0]].$$

The functionality is defined as follows:


$$z \in T_n \implies [S[n-1:0]] = z$$

$$z \in T_n \iff OVF = 0$$

$$z < 0 \iff NEG = 1.$$

We denote a two's-complement adder/subtractor by $ADD-SUB(n)$.

 An implementation of an $\text{ADD-SUB}(n)$



Claim

The implementation of $\text{ADD-SUB}(n)$ is correct.

ב. (7 נק') המספר המיוצג בשיטת משלים ל-2 על ידי $A[n-1:0]$ הוא:


$$[A[n-1:0]] \triangleq -2^{n-1} \cdot A[n-1] + \sum_{i=0}^{n-2} A[i] \cdot 2^i$$

ציירו סכימה של מעגל שבהינתן מחרוזת $A[n-1:0] \in \{0,1\}^n$, פולט מחרוזת $B[n:0] \in \{0,1\}^{n+1}$ כך ש:

$$[B] = -[A]$$

שימו לב שבקלט יש n ביטים ובפלט יש $n+1$ ביטים.

Exam Fall-2011, Question B - Answer

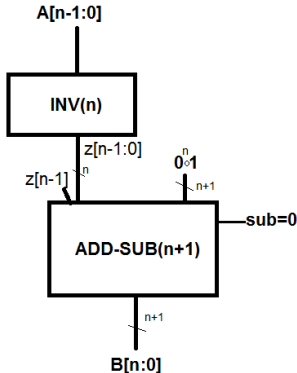

Explanation

The duplication of $z[n-1]$ extends the sign of z for $n+1$ bits. The circuit will never output overflow and its correctness is according to the claim proved in class $-[A] = [\bar{A}] + 1$.

Exam Fall-2014 Moed B, Question 1

שאלה 1 – מעגל צירופי (30 נק')

המעגל C_n מוגדר לפי המפרט הבא (הניחו כי $n > 5$):

קלט: $x[n-1:0] \in \{0,1\}^n$

פלט: $y[n-1:0] \in \{0,1\}^n$, $ovf, neg \in \{0,1\}$

פונקציונליות: נגדיר את z באופן הבא: $z \triangleq 31 \cdot [x[n-1:0]]$ (31 כפול המספר המיוצג על x בשיטת משלים ל-2)

ההגדרה החלקית של y היא: $if\ z \in \{-2^{n-1}, \dots, 2^{n-1} - 1\}$ then $[y] = [z]$

ההגדרות של ovf, neg הן:

$$neg \triangleq \begin{cases} 1 & if\ z < 0 \\ 0 & otherwise \end{cases}$$


$$ovf \triangleq \begin{cases} 1 & if\ z \notin \{-2^{n-1}, \dots, 2^{n-1} - 1\} \\ 0 & if\ z \in \{-2^{n-1}, \dots, 2^{n-1} - 1\} \end{cases}$$

א. (60%) ציירו סכמת בלוקים של המעגל C_n . (עם עדיפות להשהיה קטנה על פני מחיר נמוך)

ג. (15%) חשבו את מחיר המעגל C_n כפי שמימשם אותו בסעיף א.

ד. (15%) חשבו את השהיית המעגל C_n כפי שמימשם אותו בסעיף א.

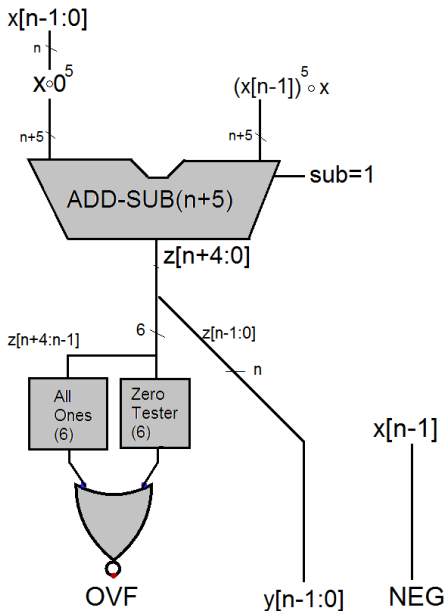
Exam Fall-2014 Moed B, Question 1 - Answer



Synchronous Circuits

Synchronous Circuits - Attributes

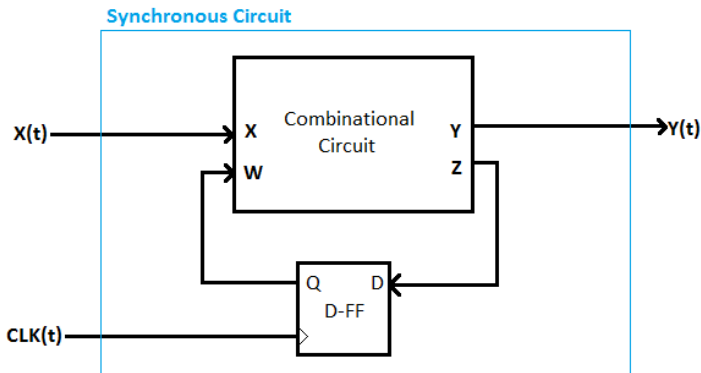- 1 Consist of combinational circuits and flip-flops (FFs)
- 2 Can contain cycles, as long as the underlying combinational circuits are still acyclic.
- 3 Must contain a special CLK input, which should be fed to all FFs



Synchronous Circuits - Time

- 1 We introduce **discrete time**
- 2 The time is dictated by a very special signal $\mathbf{CLK} \in \{0,1\}$. This signal is given automatically, you don't have to worry about generating it. Just don't forget to connect it to the required elements (FFs).
- 3 Each **rising-edge** of CLK advances the time to the next clock cycle.
- 4 The inputs are now **time-dependent**: No more X, Y, Z . In synchronous circuits we deal with $X(t), Y(t), Z(t)$. The "user" of a synchronous circuit can change these inputs every clock cycle.
- 5 Don't confuse between the time indices and the string indices.

Example

- $X[i](t)$ is the value of the binary string X at index i at time t .
- $X[2](3)$ is the value of the binary string X at index 2 at time 3.


Edge-triggered flip-flop

Definition (edge-triggered flip-flop)

Inputs: $D(t)$ and a clock CLK.

Output: $Q(t)$.

 Functionality: If $D(t)$ is stable during the critical segment C_i , then $Q(t) = D(t_i)$ during the interval $(t_i + t_{pd}, t_{i+1} + t_{cont})$.




Cost of a Flip-Flop

The FFs have their own cost which is typically much more expensive than combinational gates. Hence, a cost of a synchronous circuit will consist of combinational price + FF price.

Timing diagram of a Flip Flop

 - The x -axis corresponds to time.
- A green interval means that the signal is stable during this interval.
- A red interval means that the signal may be instable.
- In order to sample the $D(t)$ by the FF, $D(t)$ must be stable during the C_i , or in other words:
- In order to sample the $D(t)$ by the FF, $D(t)$ must be stable t_{su} seconds before the rising edge and until t_{hold} after it.



The Zero Delay Model

Simplified model for specifying and simulating the functionality of circuits with flip-flops.

- ① Transitions of all signals are instantaneous.
- ② Combinational gates: $t_{pd} = t_{cont} = 0$.
- ③ Flip-flops satisfy:

$$t_{su} = t_{i+1} - t_i,$$
$$t_{hold} = t_{cont} = t_{pd} = 0.$$

- ④ This allows us to specify the functionality of a flip-flop in the zero delay model as follows:

$$Q(t+1) = D(t).$$

Clock enabled flip-flops (zero-delay model)

Definition

A clock enabled flip-flop is defined as follows.

Inputs: $D(t), CE(t) \in \{0, 1\}$ and a clock CLK.

Output: $Q(t) \in \{0, 1\}$.

Functionality:

$$Q(t+1) = \begin{cases} D(t) & \text{if } CE(t) = 1 \\ Q(t) & \text{if } CE(t) = 0. \end{cases}$$

