

Digital Logic Systems

Recitation 12: Synchronous Circuits: Finite State Machines, Analysis and Synthesis. ISA of DLX

Guy Even Moti Medina

School of Electrical Engineering Tel-Aviv Univ.

June 3, 2019

Definition

A *finite state machine* (FSM) is a 6-tuple $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$, where

- Q is a set of *states*.
- Σ is the alphabet of the input.
- Δ is the alphabet of the output.
- $\delta : Q \times \Sigma \rightarrow Q$ is a *transition function*.
- $\lambda : Q \times \Sigma \rightarrow \Delta$ is an *output function*.
- $q_0 \in Q$ is an *initial state*.

The Canonic Form of a Synchronous Circuit

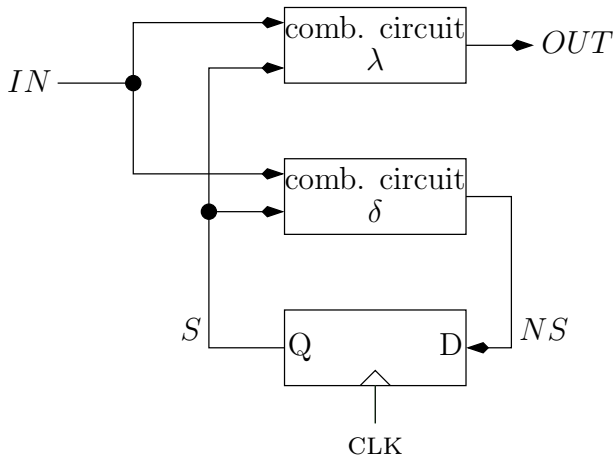


Figure: A synchronous circuit in canonic form.

Synthesis and Analysis

Two tasks are often associated with synchronous circuits:


- ① **Analysis:** given a synchronous circuit S , describe its functionality by an FSM.
- ② **Synthesis:** given an FSM \mathcal{A} , design a synchronous circuit S that implements \mathcal{A} .

Synthesis and Analysis

Two tasks are often associated with synchronous circuits:

- 1 **Analysis:** given a synchronous circuit S , describe its functionality by an FSM.
- 2 **Synthesis:** given an FSM \mathcal{A} , design a synchronous circuit S that implements \mathcal{A} .

 This is somewhat similar to what we already did:



The task of analyzing a synchronous circuit S is carried out as follows.

- ① Define the FSM $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$ as follows.
 - ① The set of **states** is $Q \triangleq \{0, 1\}^k$, where k denotes the number of flip-flops in S .
 - ② Define the **initial state** q_0 to be the initial outputs of the flip-flops.
 - ③ $\Sigma = \{0, 1\}^\ell$, where ℓ denotes the number of **input** gates in S .
 - ④ $\Delta = \{0, 1\}^r$, where r denotes the number of **output** gates in S .
 - ⑤ **Transform** S to a functionally equivalent synchronous circuit \tilde{S} in **canonic form**. Compute the truth tables of the combinational circuits λ and δ . Define the **Boolean functions** according to these **truth tables**.

Given an FSM $\mathcal{A} = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$, the task of designing a synchronous circuit S that implements \mathcal{A} is carried out as follows.

- 1 Encode Q, Σ and Δ by binary strings. Formally, let f, g, h denote one-to-one functions, where

$$f : Q \rightarrow \{0, 1\}^k$$

$$g : \Sigma \rightarrow \{0, 1\}^\ell$$

$$h : \Delta \rightarrow \{0, 1\}^r.$$

- 2 Design a combinational circuit C_δ that implements the (partial) Boolean function $B_\delta : \{0, 1\}^k \times \{0, 1\}^\ell \rightarrow \{0, 1\}^k$ defined by

$$B_\delta(f(x), g(y)) \triangleq f(\delta(x, y)), \text{ for every } (x, y) \in Q \times \Sigma.$$

- ③ Design a combinational circuit C_λ that implements the (partial) Boolean function $B_\lambda : \{0,1\}^k \times \{0,1\}^\ell \rightarrow \{0,1\}^r$ defined by

$$B_\lambda(f(x), g(z)) \triangleq f(\lambda(x, z)), \text{ for every } (x, z) \in Q \times \Sigma.$$

- ④ Let S denote the synchronous circuit in canonic form constructed from k flip-flops and the combinational circuits C_δ for the next state and C_λ for the output.

Synthesis - how to encode the states?


Let S denote the synchronous circuit in canonic form constructed from k flip-flops and the combinational circuits C_δ for the next state and C_λ for the output.

The description of the encoding step leaves a great deal of freedom. Since $|\{0,1\}^k| \geq |Q|$, it follows that $k \geq \log_2 |Q|$, and similar bounds apply to ℓ and r . However, it is not clear that using the smallest lengths is the best idea. Certain encodings lead to more complicated Boolean functions B_δ and B_λ . Thus, the question of selecting a “good” encoding is a very complicated task, and there is no simple solution to this problem.


Analysis Question

Analyze the circuit shift-register(2)

 i.e. draw a state diagram of the corresponding FSM.



(a) Shift-Reg(2)

 

(b) FSM(Shift-Reg(2)) Which is an important graph called De Bruijn Graph

Synthesis Question

Design a synchronous circuit S that satisfies the following:

Input: $x(t), y(t) \in \{0, 1\}$, for every clock cycle t .

Output: $EQ(t), LT(t), GT(t) \in \{0, 1\}$, for every clock cycle t .

Functionality: Let $X_t \triangleq \langle x(t), \dots, x(0) \rangle$, $Y_t \triangleq \langle y(t), \dots, y(0) \rangle$

For every clock cycle $t \geq 0$:

$$EQ(t) = \begin{cases} 1, & \text{if } X_t = Y_t, \\ 0, & \text{otherwise.} \end{cases}$$

$$LT(t) = \begin{cases} 1, & \text{if } X_t < Y_t, \\ 0, & \text{otherwise.} \end{cases}$$

$$GT(t) = \begin{cases} 1, & \text{if } X_t > Y_t, \\ 0, & \text{otherwise.} \end{cases}$$

- 1 **FSM(S)** - Define the finite state machine $FSM(S) = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$ that satisfies the specification.
- 2 **Synthesize S** - Implement S by synthesizing $FSM(S)$.

FSM - Understand the required behavior

5	4	3	2	1	0	t	
0	0	1	1	1	0	$x(t)$	Inputs
0	1	1	0	1	0	$y(t)$	
14	14	14	6	2	0	$X_t \triangleq \langle x(t), \dots, x(0) \rangle$	Interpretation
26	26	10	2	2	0	$Y_t \triangleq \langle y(t), \dots, y(0) \rangle$	
0	0	0	0	1	1	EQ(t)	Outputs
1	1	0	0	0	0	LT(t)	
0	0	1	1	0	0	GT(t)	

- Observation 1: The inputs are streamed from the LSB \Rightarrow MSB

FSM - Understand the required behavior

5	4	3	2	1	0	t	
0	0	1	1	1	0	$x(t)$	Inputs
0	1	1	0	1	0	$y(t)$	
14	14	14	6	2	0	$X_t \triangleq \langle x(t), \dots, x(0) \rangle$	Interpretation
26	26	10	2	2	0	$Y_t \triangleq \langle y(t), \dots, y(0) \rangle$	
0	0	0	0	1	1	EQ(t)	Outputs
1	1	0	0	0	0	LT(t)	
0	0	1	1	0	0	GT(t)	

- Observation 1: The inputs are streamed from the LSB \Rightarrow MSB
- Observation 2: Outputs at time t depend on inputs at time t .

FSM - Understand the required behavior

5	4	3	2	1	0	t	
0	0	1	1	1	0	$x(t)$	Inputs
0	1	1	0	1	0	$y(t)$	
14	14	14	6	2	0	$X_t \triangleq \langle x(t), \dots, x(0) \rangle$	Interpretation
26	26	10	2	2	0	$Y_t \triangleq \langle y(t), \dots, y(0) \rangle$	
0	0	0	0	1	1	EQ(t)	Outputs
1	1	0	0	0	0	LT(t)	
0	0	1	1	0	0	GT(t)	

- Observation 1: The inputs are streamed from the LSB \Rightarrow MSB
- Observation 2: Outputs at time t depend on inputs at time t .
- What will our circuit need to “memorize” to be able to determine the output at time t ?

FSM - Understand the required behavior

5	4	3	2	1	0	t	
0	0	1	1	1	0	$x(t)$	Inputs
0	1	1	0	1	0	$y(t)$	
14	14	14	6	2	0	$X_t \triangleq \langle x(t), \dots, x(0) \rangle$	Interpretation
26	26	10	2	2	0	$Y_t \triangleq \langle y(t), \dots, y(0) \rangle$	
0	0	0	0	1	1	EQ(t)	Outputs
1	1	0	0	0	0	LT(t)	
0	0	1	1	0	0	GT(t)	

- Observation 1: The inputs are streamed from the LSB \Rightarrow MSB
- Observation 2: Outputs at time t depend on inputs at time t .
- What will our circuit need to “memorize” to be able to determine the output at time t ?
 - All the input bits from time 0? Namely $\{x(\tau), y(\tau)\}_{\tau=0}^{t-1}$

FSM - Understand the required behavior

5	4	3	2	1	0	t	
0	0	1	1	1	0	$x(t)$	Inputs
0	1	1	0	1	0	$y(t)$	
14	14	14	6	2	0	$X_t \triangleq \langle x(t), \dots, x(0) \rangle$	Interpretation
26	26	10	2	2	0	$Y_t \triangleq \langle y(t), \dots, y(0) \rangle$	
0	0	0	0	1	1	EQ(t)	Outputs
1	1	0	0	0	0	LT(t)	
0	0	1	1	0	0	GT(t)	

- Observation 1: The inputs are streamed from the LSB \Rightarrow MSB
- Observation 2: Outputs at time t depend on inputs at time t .
- What will our circuit need to “memorize” to be able to determine the output at time t ?
 - All the input bits from time 0? Namely $\{x(\tau), y(\tau)\}_{\tau=0}^{t-1}$
Bad, the required information grows with time

FSM - Understand the required behavior

5	4	3	2	1	0	t	
0	0	1	1	1	0	$x(t)$	Inputs
0	1	1	0	1	0	$y(t)$	
14	14	14	6	2	0	$X_t \triangleq \langle x(t), \dots, x(0) \rangle$	Interpretation
26	26	10	2	2	0	$Y_t \triangleq \langle y(t), \dots, y(0) \rangle$	
0	0	0	0	1	1	EQ(t)	Outputs
1	1	0	0	0	0	LT(t)	
0	0	1	1	0	0	GT(t)	

- Observation 1: The inputs are streamed from the LSB \Rightarrow MSB
- Observation 2: Outputs at time t depend on inputs at time t .
- What will our circuit need to “memorize” to be able to determine the output at time t ?
 - All the input bits from time 0? Namely $\{x(\tau), y(\tau)\}_{\tau=0}^{t-1}$
Bad, the required information grows with time
 - Just the relation between X_{t-1} and Y_{t-1} .

FSM - Understand the required behavior

5	4	3	2	1	0	t	
0	0	1	1	1	0	$x(t)$	Inputs
0	1	1	0	1	0	$y(t)$	
14	14	14	6	2	0	$X_t \triangleq \langle x(t), \dots, x(0) \rangle$	Interpretation
26	26	10	2	2	0	$Y_t \triangleq \langle y(t), \dots, y(0) \rangle$	
0	0	0	0	1	1	EQ(t)	Outputs
1	1	0	0	0	0	LT(t)	
0	0	1	1	0	0	GT(t)	


- Observation 1: The inputs are streamed from the LSB \Rightarrow MSB
- Observation 2: Outputs at time t depend on inputs at time t .
- What will our circuit need to “memorize” to be able to determine the output at time t ?
 - All the input bits from time 0? Namely $\{x(\tau), y(\tau)\}_{\tau=0}^{t-1}$
 Bad, the required information grows with time
 - Just the relation between X_{t-1} and Y_{t-1} .
 Good, only 3 options “equal” “less than” “greater than”

FSM - Declare the states and the encodings

- Let's Describe the $FSM(S) = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$ and also provide the encodings:
 - $Q \triangleq \{0, 1\}^2$ - the states
 - 00 for $X_t = Y_t$ (The "EQ" state)
 - 01 for $X_t < Y_t$ (The "LT" state)
 - 10 for $X_t > Y_t$ (The "GT" state)
 - $\Sigma \triangleq \{0, 1\}^2$ - the input alphabet.
The two inputs $x(t), y(t)$ are simply concatenated together.
 - $\Delta \triangleq \{0, 1\}^3$ - the output alphabet
 - 100 for EQ(t)
 - 010 for LT(t)
 - 001 for GT(t)
 - q_0 is 00, (The equality state)

FSM - State Diagram

 


- Let's Describe the $FSM(S) = \langle Q, \Sigma, \Delta, \delta, \lambda, q_0 \rangle$
- δ - state-transfer function, receives the current input and the current state and returns the next state.
- λ - output-function, receives the current input and the current state and returns the current output.
- We describe the two functions using a **state diagram**:



Synthesis - Recovering truth table of δ and λ from FSM


Translate each state into 4 rows of the table.

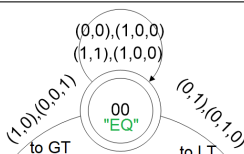Note that $S[1:0] = 11$ is an inaccessible state.

Current State	S[1]	S[0]	x	y	NS[1]	NS[0]	EQ	LT	GT
	0	0	0	0	0	0	1	0	0
	0	0	0	1	0	1	0	1	0
	0	0	1	0	1	0	0	0	1
	0	0	1	1	0	0	1	0	0
	0	1	0	0	0	1	0	1	0
	0	1	0	1	0	1	0	1	0
	0	1	1	0	1	0	0	0	1
	0	1	1	1	0	1	0	1	0
	1	0	0	0	1	0	0	0	1
	1	0	0	1	0	1	0	1	0
	1	0	1	0	1	0	0	0	1
	1	0	1	1	1	0	0	0	1


Synthesis - Implementing C_δ (skipping truth table)

- The C_δ - state-transfer circuit receives the $IN = x(t) \circ y(t)$ and the current state S and outputs the next state NS .
- We can derive the C_δ formulas **directly** from the FSM(S):
 $NS = 00 \Leftrightarrow S = 00 \text{ and } x(t) = y(t)$
 $NS = 01 \Leftrightarrow x(t) < y(t) \text{ or } (S = 01 \text{ and } x(t) = y(t))$
 $NS = 10 \Leftrightarrow x(t) > y(t) \text{ or } (S = 10 \text{ and } x(t) = y(t))$

 

Synthesis - Implementing C_δ

- We can derive the C_δ formulas from the FSM(S):
 $NS = 00 \Leftrightarrow S = 00$ and $x(t) = y(t)$
 $NS = 01 \Leftrightarrow x(t) < y(t)$ or $(S = 01$ and $x(t) = y(t))$
 $NS = 10 \Leftrightarrow x(t) > y(t)$ or $(S = 10$ and $x(t) = y(t))$
- We further provide the boolean function per each flip-flop:
 $NS[0] = \bar{x} \cdot y + (\overline{S[1]} \cdot \underline{S[0]} \cdot NXOR(x, y))$
 $NS[1] = x \cdot \bar{y} + (S[1] \cdot \underline{S[0]} \cdot NXOR(x, y))$

 


Synthesis - Implementing C_λ (skipping truth table)

- The C_λ - output circuit receives the $IN = x(t) \circ y(t)$ and the current state S and generates outputs $EQ(t), LT(t), GT(t)$.
- We can derive the C_λ formulas **directly** from the $FSM(S)$:

$$EQ = 1 \Leftrightarrow S = 00 \text{ and } x(t) = y(t)$$

$$LT = 1 \Leftrightarrow x(t) < y(t) \text{ or } (S = 01 \text{ and } x(t) = y(t))$$
 
$$GT = 1 \Leftrightarrow x(t) > y(t) \text{ or } (S = 10 \text{ and } x(t) = y(t))$$




Synthesis - Implementing C_λ

- We can derive the C_λ formulas from the FSM(S):
 $EQ = 1 \Leftrightarrow S = 00$ and $x(t) = y(t)$
 $LT = 1 \Leftrightarrow x(t) < y(t)$ or $(S = 01$ and $x(t) = y(t))$
 $GT = 1 \Leftrightarrow x(t) > y(t)$ or $(S = 10$ and $x(t) = y(t))$
- We further provide the boolean function per each flip-flop:

$$EQ = \overline{S[0]} \cdot \overline{S[1]} \cdot NXOR(x, y)$$


$$LT = \bar{x} \cdot y + (\overline{S[1]} \cdot S[0] \cdot NXOR(x, y))$$
 
$$GT = x \cdot \bar{y} + (S[1] \cdot \overline{S[0]} \cdot NXOR(x, y))$$



Synthesis - Putting it all together into S

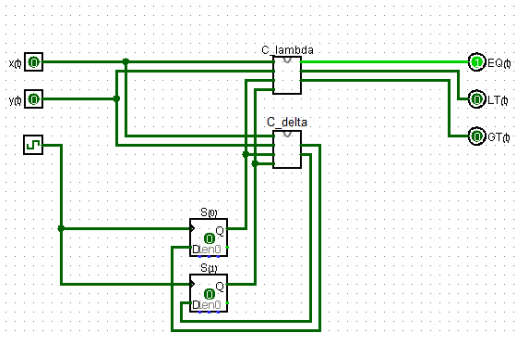- Instantiate the C_δ and the C_λ circuits.
- Add k flip-flops for the state storage.



RESAb3 software contains the **text editor** for writing the assembly code, and the **DLX simulator** for running it.

- ① Open the Resa program and choose a text editor.
- ② Write a program in a text editor, and compile it to ensure that it has no compilation errors. This should generate the “.cod” file with the machine code.
- ③ File→New to open simulator window.
- ④ In the simulator window File→Open COD to load the machine code.
- ⑤ Simulator→Add Watch to observe a particular memory cell.
- ⑥ Run→Run Until Halt to execute the whole program